

## Arithmetic in Log-Depth Circuits

In this lecture we show how small-depth circuit can implement various fundamental arithmetic operations.

### 1 Addition

Input: Two  $n$ -bit Integers  $X, Y \in \{0, 1\}^n$ .

Output:  $X + Y \in \{0, 1\}^{n+1}$ .

**Theorem 1.** *Addition is computable by polynomial-size circuits of unbounded fan-in and depth  $O(1)$ . In particular, addition is computable by fan-in 2 circuits of depth  $O(\log n)$ .*

*Proof.* The difficulty in proving the above theorem is that the computation of the carries appears sequential. Note however that if the carries  $c_n, \dots, c_1 \in \{0, 1\}$  are given then each bit of  $X + Y$  can be computed by circuits of size  $O(1)$  (and hence depth  $O(1)$ ). Specifically  $(X + Y)_1 = X_1 + Y_1 + c_1$  where here “+” denotes bit XOR, and similarly for the other bits.

Our approach is to compute all the carries in parallel using *carry look-ahead*. Specifically we note that the  $i$ -th carry is 1 if and only if there is some less significant position  $j < i$  where the carry is generated and it is propagated up to  $i$ . This can be written as

$$c_i = 1 \iff \bigvee_{j < i} \left( X_j = 1 \wedge Y_j = 1 \bigwedge_{k=j+1}^{i-1} (X_k = 1 \vee Y_k = 1) \right).$$

The above is an unbounded fan-in circuit of size  $\text{poly}(n)$  and depth  $O(1)$ . By the claim from last lecture, this can be implemented by a fan-in 2 circuit of depth  $O(\log n)$ .  $\square$

### 2 Iterated Addition

Input:  $n$   $n$ -bit integers  $x_1, \dots, x_n \in \{0, 1\}^n$ .

Output:  $\sum x_i$ .

If we are able to compute iterated addition in depth  $O(\log n)$ , then Majority can also be computed in depth  $O(\log n)$ .

**Theorem 2.** *Iterated Addition is computable by fan-in 2 circuits of depth  $O(\log n)$ .*

*Proof.* We use the technique “2-out-of-3:” given 3 integers  $X, Y, Z$ , we compute 2 integers  $a, b$  such that

$$X + Y + Z = a + b,$$

where each bit of  $a, b$  is a function of one bit from  $X$ , one from  $Y$ , and one from  $Z$ , and thus can be computed by a circuit of constant size. If you can do this, then to compute iterated addition we construct a tree of logarithmic depth to reduce the original sum to a sum of 2 terms, which we add as explained before.

Proof of trick:  $X_i + Y_i + Z_i \leq 3$ , so  $a_i$  will get the least significant bit,  $b_{i+1}$  will get the most significant one. Note that  $a_i$  is the XOR  $X_i + Y_i + Z_i \in \{0, 1\}$ , while  $b_{i+1}$  is the majority of  $X_i, Y_i, Z_i$ .  $\square$

### 3 Multiplication

Input:  $X, Y$   $n$ -bit integers,  
Output:  $X \cdot Y$   $2n$ -bit integer.

**Theorem 3.** *Multiplication is computable by fan-in 2 circuits of depth  $O(\log n)$ .*

*Proof.* “Shift and Add:”  $X \cdot Y = \sum_i (X \cdot 2^i \cdot b_i)$ . Each term  $(X \cdot 2^i \cdot b_i)$  is easily computable in constant depth, since multiplication by  $2^i$  is just a bit shift. Then we apply iterated addition.  $\square$

### 4 Division

Input:  $X$   $n$ -bit integer,  
Output:  $1/X$  to within  $n$  bits of precision.  
Note: if we can compute  $1/X$ , can compute  $Y/X$  as  $Y \cdot 1/X$ .

To divide, we are going to power.

**Theorem 4** (Powering). *Given  $X$   $n$ -bit integer, we can compute  $X^n$  by fan-in 2 depth  $O(\log n)$  circuits.*

**Theorem 5** (Division). *Given  $X \geq 0$   $n$ -bit integer, we can compute  $1/X$  to within  $n$  bits of precision by fan-in 2 circuits of depth  $O(\log n)$ .*

*Proof of Theorem 5 assuming Theorem 4.* Given  $X$ , determine  $j$  such that  $2^j \leq X < 2^{j+1}$ , let  $U := 1 - X/2^{j+1} \in (0, 1/2)$ . Using iterated addition and multiplication, compute

$$\begin{aligned} 2^{-(j+1)}(1 + U + U^2 + \dots + U^n) &= 2^{-(j+1)} \cdot \frac{1 - U^{n+1}}{1 - U} \\ &= 2^{-(j+1)} \cdot \frac{1 - U^{n+1}}{X \cdot 2^{-(j+1)}} = \frac{1}{X} - \frac{U^{n+1}}{X} = \frac{1}{X} \pm 2^{-n}. \end{aligned}$$

$\square$

To power (Theorem 4) we use various tools from number theory.

## 5 Tools from number theory

**Theorem 6** (Chinese Remainder Theorem). *Let  $p_1, \dots, p_l$  be distinct primes and  $p' := \prod_i p_i$ .  $\mathbb{Z}_{p'}$  is isomorphic to  $\mathbb{Z}_{p_1} \times \dots \times \mathbb{Z}_{p_l}$ .*

*The forward direction of the isomorphism is given by  $x \in \mathbb{Z}_{p'} \rightarrow (x \bmod p_1, x \bmod p_2, \dots, x \bmod p_l) \in \mathbb{Z}_{p_1} \times \dots \times \mathbb{Z}_{p_l}$ .*

*For the converse direction, we claim that there exist integers  $e_1, \dots, e_l \leq \text{poly}(p')$  such that  $(x \bmod p_1, x \bmod p_2, \dots, x \bmod p_l) \in \mathbb{Z}_{p_1} \times \dots \times \mathbb{Z}_{p_l} \rightarrow x := \sum_{i=1}^l e_i \cdot (x \bmod p_i)$ .*

Each integer  $e_i$  is 0 mod  $p_j$  for  $j \neq i$ , is 1 mod  $p_i$ , and can be found using the extended euclidean algorithm.

For example,  $\mathbb{Z}_6 \simeq \mathbb{Z}_2 \times \mathbb{Z}_3$ , and  $2 + 3 = 5 \rightarrow (0, 2) + (1, 0) = (1, 2)$ .

We recall the following celebrated result on the density of prime numbers, a weak version of which will be proved in the next lecture.

**Theorem 7** (Prime number theorem).  $\lim_{n \rightarrow \infty} (\text{Number of primes} \leq n) / (n / \log_e n) = 1$ .

## 6 Powering

Input:  $X \in \{0, 1\}^n$ . Output:  $X^n$ .

*Beginning of the proof of Theorem 4 that powering has fan-in 2 circuits of depth  $O(\log n)$ . Let  $l := n^3$ . We use the following algorithm:*

1. Compute  $(X \bmod p_1, X \bmod p_2, \dots, X \bmod p_l)$ ,
2. Compute  $(X^n \bmod p_1, \dots, X^n \bmod p_l)$ ,
3. Compute  $X^n$ .

*Correctness:* Observe  $X^n \leq 2^{n^2}$ , thus the correctness follows from the Chinese remaindering theorem if  $p' := \prod_{i=1}^l p_i \geq 2^{n^2}$ , which follows immediately by our choice of  $l$  and the fact that each prime is at least 2.

In the next class we will show that the above algorithm can be implemented by log-depth circuits.  $\square$